

Digital Logic got BORING !!!


# Un-Boring Digital Logic !!!

# Tri-State Buffer

# Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire

Tristate  
Buffer

 

$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1

Figure 2.40 Tristate buffer

- **Floating signal (Z):** Signal that is not driven by any circuit
  - Open circuit, floating wire


# Example: Use of Tri-State Buffers

---

- Imagine a wire connecting the CPU and memory
    - At any time only the CPU or the memory can place a value on the wire, both not both
    - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time
-


# Example Design with Tri-State Buffers

---

 


# Another Example

---

 


# Multiplexer Using Tri-State Buffers

 


$$Y = D_0 \bar{S} + D_1 S$$

**Figure 2.56** Multiplexer using tristate buffers

 



# Barrel Shifter Using Tri-State Buffers

 

# 4-valued logic

---

<b>buf</b>	
input	output
0	0
1	1
x	x
z	x

<b>not</b>	
input	output
0	1
1	0
x	x
z	x

---

# 4-valued logic

---

<b>and</b>	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

<b>or</b>	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

<b>xor</b>	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

<b>nand</b>	0	1	x	z
0	1	1	1	1
1	1	0	x	x
x	1	x	x	x
z	1	x	x	x

<b>nor</b>	0	1	x	z
0	1	0	x	x
1	0	0	0	0
x	x	0	x	x
z	x	0	x	x

<b>xnor</b>	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

---

# 4-valued logic

---

bufif0		control input			
		0	1	x	z
data input	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

bufif1		control input			
		0	1	x	z
data input	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

- The L and H symbols have a special meaning.
    - The **L symbol** means that the output has 0 or z value.
    - The **H symbol** means that the output has 1 or z value.
    - Any transition to H or L is treated as a transition to x.
-

# Tradeoffs in Circuit Design

# Circuit Design is a Tradeoff Between:

---

- Area

- Circuit **area** is proportional to the **cost** of the device

- Speed / Throughput

- We want **faster**, more **capable** circuits

- Power / Energy


- Mobile devices need to work with a **limited** power supply
- High performance devices **dissipate** more than  $100\text{W}/\text{cm}^2$

- Design Time

- Designers are **expensive** in time and money
  - The **competition** will not wait for you
-

# Requirements and Goals Depend On Application

---

 

# Circuit Timing

---

- Until now, we investigated **logical functionality**
  - What about **timing**?
    - How **fast** is a circuit?
    - How can we make a circuit **faster**?
    - What happens if we run a circuit **too fast**?
  - A design that is logically correct can still **fail** because of real-world **implementation issues**!
-





# Combinational Circuit Timing
  
# Digital Logic Abstraction


---

- **“Digital logic”** is a convenient **abstraction**
  - Output changes **immediately** with the input



 
# Combinational Circuit Delay

- In reality, **outputs** are **delayed** from **inputs**
  - Transistors take a finite amount of time to switch



# Real Inverter Delay Example

 

# Circuit Delay and Its Variation


---

- Delay is fundamentally caused by
    - **Capacitance** and **resistance** in a circuit
    - Finite **speed of light** (not so fast on a nanosecond scale!)
  - **Anything** affecting these quantities can change delay:
    - **Rising** (i.e., 0 -> 1) vs. **falling** (i.e., 1 -> 0) inputs
    - Different **inputs** have different **delays**
    - Changes in **environment** (e.g., temperature)
    - **Aging** of the circuit
  - We have a **range of possible delays** from input to output
-


# Delays from Input to Output

- **Contamination delay ( $t_{cd}$ ):** delay until Y **starts** changing
- **Propagation delay ( $t_{pd}$ ):** delay until Y **finishes** changing

## Example Circuit

 


## Effect of Changing Input 'A'

 

**Cross-hatching  
means value is**
 
# Calculating Long/Short Paths

- We care about **both** the **longest** and **shortest** paths in a circuit





- **Critical (Longest) Path:**

$$t_{pd} = 2 t_{pd\_AND} + t_{pd\_OR}$$

- **Shortest Path:**

$$t_{cd} = t_{cd\_AND}$$
  
# Example $t_{pd}$ for a Real NAND-2 Gate



Symbol	Parameter	Conditions	25 °C			−40 °C to +125 °C		Unit
			Min	Typ	Max	Max (85 °C)	Max (125 °C)	
74HC00								
t <sub>pd</sub>	propagation delay	nA, nB to nY; see <a href="#">Figure 6</a> <a href="#">[1]</a>						
		V <sub>CC</sub> = 2.0 V	-	25	-	115	135	ns
		V <sub>CC</sub> = 4.5 V	-	9	-	22	27	ns
		V <sub>CC</sub> = 5.0 V; C <sub>L</sub> = 15 pF	-	7	-	-	-	ns
		V <sub>CC</sub> = 6.0 V	-	7	-	20	23	ns

- Heavy **dependence** on **voltage** and **temperature**!



# Example Worst-Case $t_{pd}$


- Two different **implementations** of a **4:1 multiplexer**

## Gate Delays

Gate	$t_{pd}$ (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

- Different designs** lead to very **different delays**


Implementation 1

 

$$\begin{aligned} t_{pd\_sy} &= t_{pd\_INV} + t_{pd\_AND3} + t_{pd\_OR4} \\ &= 30 \text{ ps} + 80 \text{ ps} + 90 \text{ ps} \\ &= \mathbf{200 \text{ ps}} \end{aligned}$$

(a)  $t_{pd\_dy} = t_{pd\_AND3} + t_{pd\_OR4}$   
 $= \mathbf{170 \text{ ps}}$

Implementation 2

 

$$\begin{aligned} t_{pd\_sy} &= t_{pd\_INV} + t_{pd\_AND2} + t_{pd\_TRI\_SY} \\ &= 30 \text{ ps} + 60 \text{ ps} + 35 \text{ ps} \\ &= \mathbf{125 \text{ ps}} \end{aligned}$$

(b)  $t_{pd\_dy} = t_{pd\_TRI\_AY}$   
 $= \mathbf{50 \text{ ps}}$

# Disclaimer: Calculating Long/Short Paths

---

- It's **not** always this easy to determine the long/short paths!
    - Not all **input transitions** affect the **output**
    - Can have **multiple different paths** from an input to output
  - In reality, circuits are **not** all built equally
    - Different instances of the **same gate** have **different delays**
    - **Wires** have **nonzero delay** (increasing with length)
    - Temperature/voltage affect circuit speeds
      - Not all circuit elements are affected the same way
      - Can even **change the critical path!**
  - Designers assume “**worst-case**” **conditions** and run many **statistical simulations** to balance yield/performance
-

# Combinational Timing Summary

---

- Circuit outputs change some time **after** the inputs change
    - Caused by finite speed of light (not so fast on a ns scale!)
    - Delay is dependent on inputs, environmental state, etc.
  - The range of possible delays is characterized by:
    - **Contamination delay ( $t_{cd}$ )**: minimum possible delay
    - **Propagation delay ( $t_{pd}$ )**: maximum possible delay
  - Delays **change** with:
    - Circuit design (e.g., topology, materials)
    - Operating conditions
-


# Output Glitches

# Glitches

---

- **Glitch:** **one** input transition causes **multiple** output transitions


## Circuit initial state

 
 
# Glitches


---

- **Glitch:** **one** input transition causes **multiple** output transitions



 
# Glitches

- **Glitch:** **one** input transition causes **multiple** output transitions


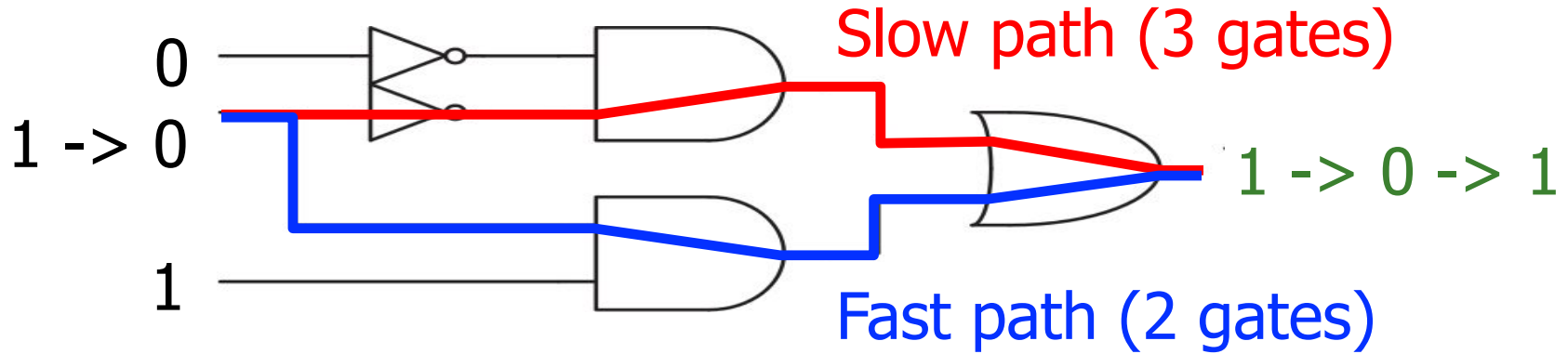
# Glitches



- **Glitch:** **one** input transition causes **multiple** output transitions





  
# Glitches

- **Glitch:** one input transition causes **multiple** output transitions



 
# Avoiding Glitches Using K-Maps

- Glitches are **visible** in **K-maps**
  - Recall: K-maps show the results of a change in a **single input**
  - A glitch occurs when **moving between prime implicants**


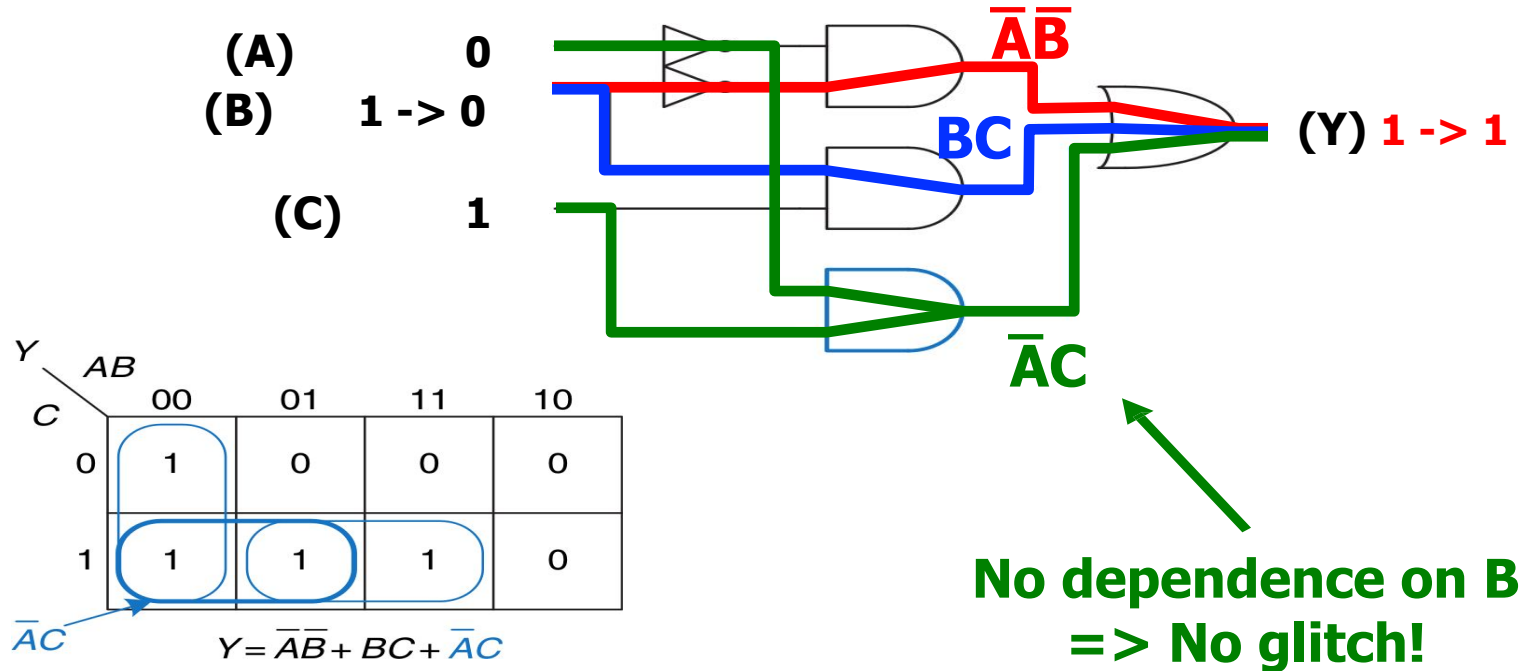
# Avoiding Glitches Using K-Maps

- We can **fix** the issue by adding in the **consensus** term
  - Ensures **no transition** between different **prime implicants**



# Avoiding Glitches

---

- **Q:** Do we **always** care about glitches?
    - **Fixing** glitches is **undesirable**
      - More chip **area**
      - More **power consumption**
      - More **design effort**
    - The circuit is **eventually** guaranteed to **converge** to the **right value** regardless of glitchiness
  - **A:** No, not always!
    - If we only care about the **long-term steady state output**, we can **safely ignore** glitches
    - Up to the **designer to decide** if glitches matter in their application
-