

Tutorial 2

DC Transients (1st order)

Problem 1

In Figure 1, the switch closes at $t=0$. Find $v_o(t)$ for $t>0$

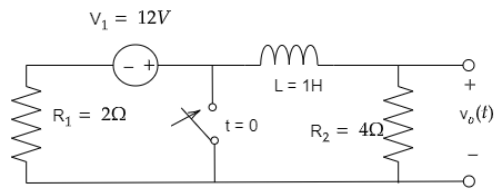


Figure 1: fig1

Problem 2

In Figure 2, find the expression for currents in the 1 mH inductor and the 90Ω resistor if the switch was on for a long time and is disconnected at time $t=0$. (Assume ideal components)

Problem 3

Consider the network shown, determine V_c , i_c and $i(t)$. Assume initial voltage of capacitor to be 0V.

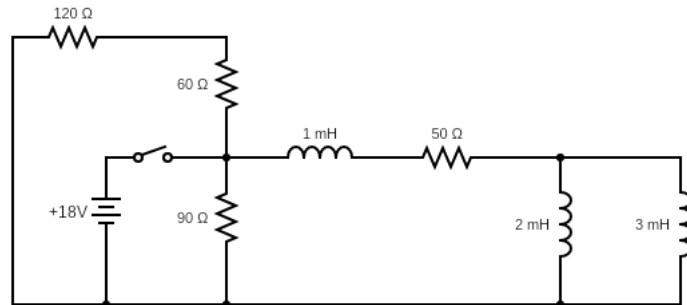


Figure 2: Circuit for problem 2

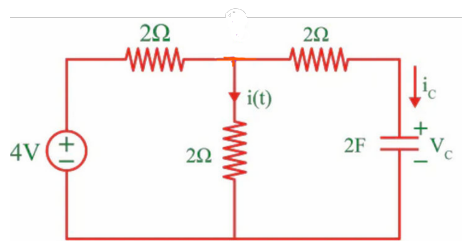


Figure 3: Circuit 3

Problem 4

Find the Steady state current in each inductor and the energy stored in them for the given circuit.

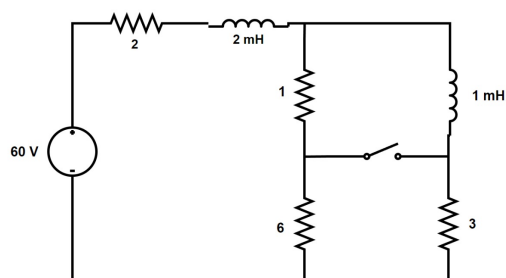


Figure 4: Circuit 4

Problem 5

Consider the following circuit. The switch is closed for a long time and it is opened at $t = 0$. Determine $i_L(0^+)$, $V(0^+)$ and $i_L(t)$ for $t > 0$

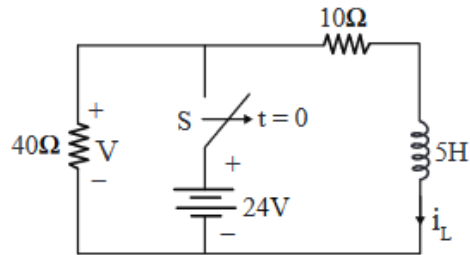


Figure 5: Circuit 5

Problem 6

Consider the following circuit. The switch is closed for a long time and it is opened at $t = 0$. Determine $V_C(0^+)$, $i(0^+)$ and $V_C(t)$ for $t > 0$

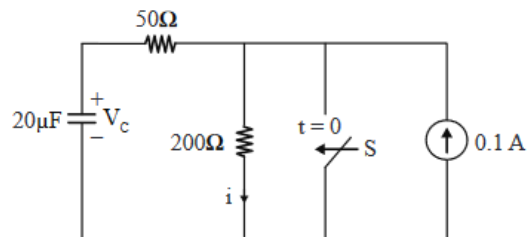


Figure 6: Circuit 6