
 


D Flip Flops


 
Homework: verify that these designs are equivalent




The problem of synchronization




The D latch with a clock for enable

 
 


Clocked D Latch

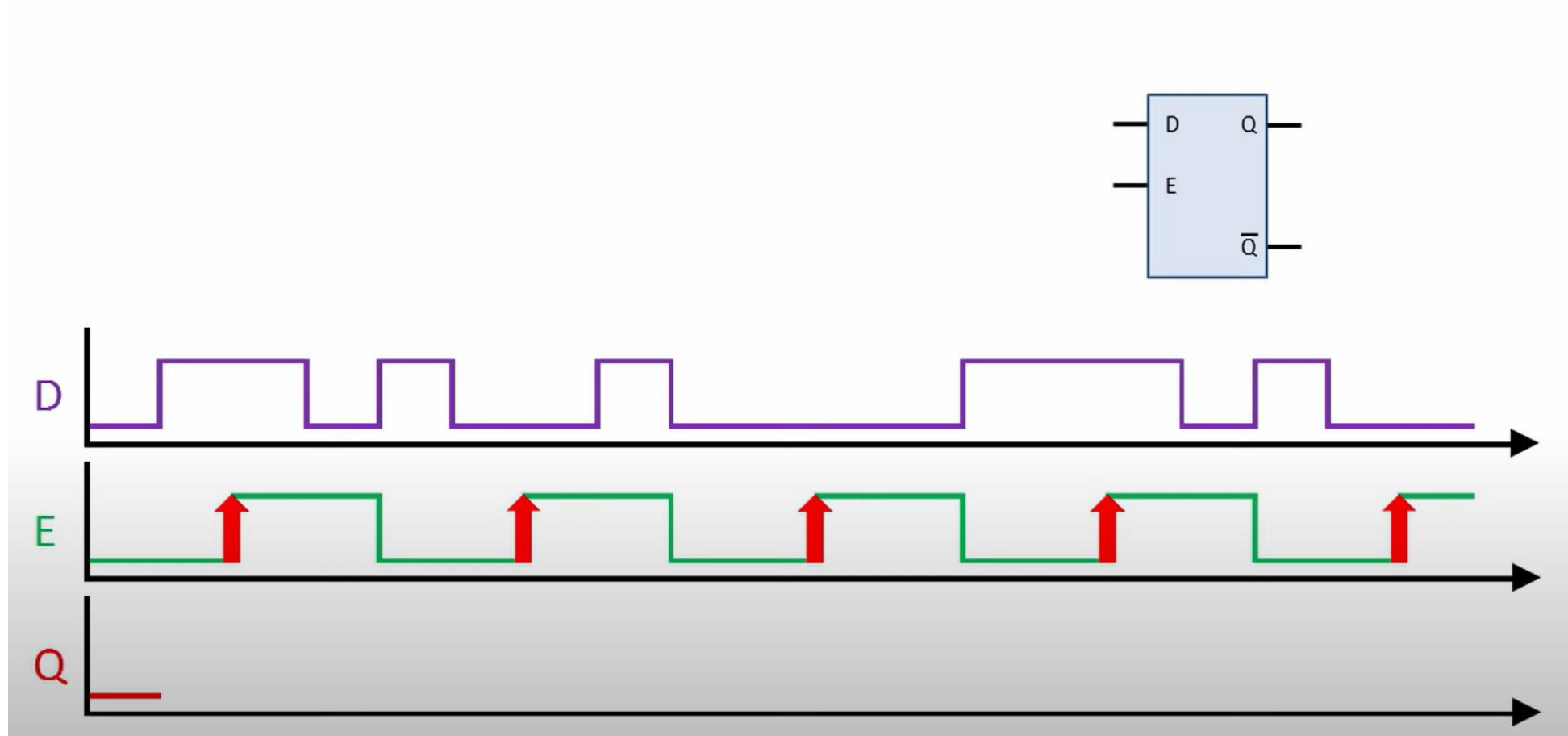




Edge detector

 

  


The Clocked D Latch

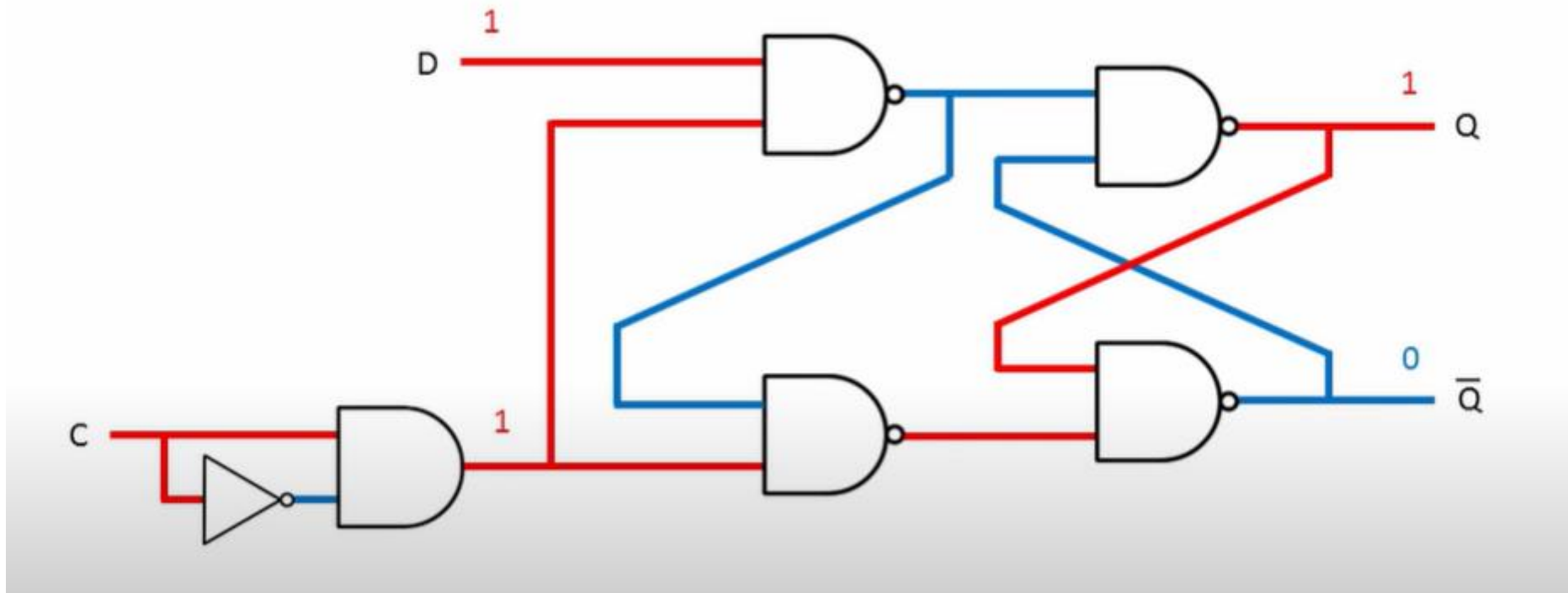

 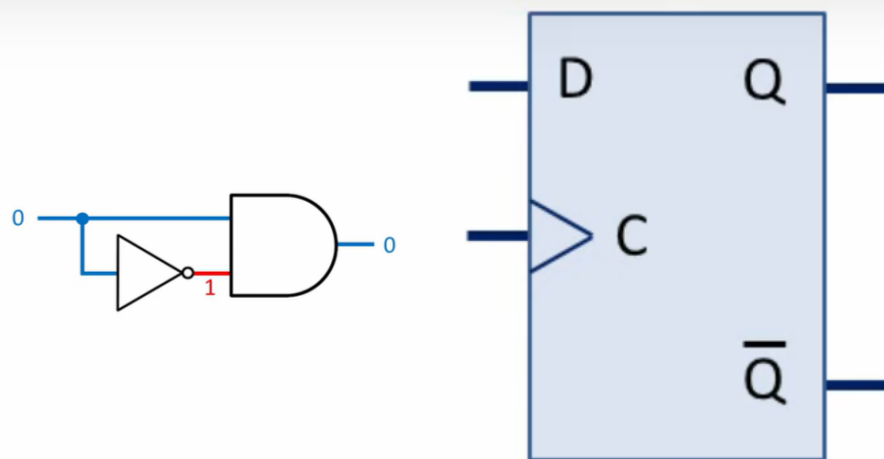

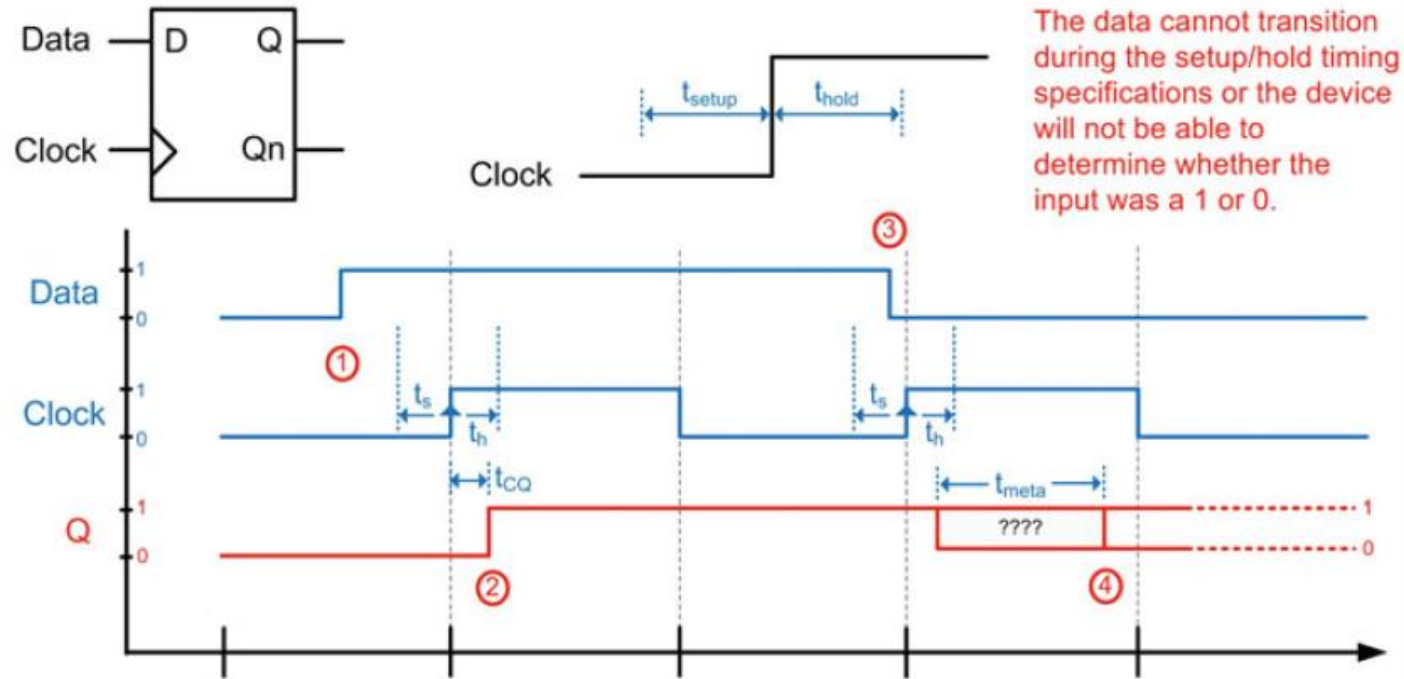Sequential Storage Device Timing Specifications



The data cannot transition during the setup/hold timing specifications or the device will not be able to determine whether the input was a 1 or 0.




① The first transition on Data from a 0 to a 1 meets the setup/hold specifications for the D-Flip-Flop. This allows the device to successfully latch in the correct value.

② The value of Data will show up on Q after the t_{cq} delay of the D-Flip-Flop.


③ The second transition on Data from a 1 to a 0 violates the setup/hold specifications for the D-Flip-Flop. This sends the device into metastability. The D-Flip-Flop will remain metastable for t_{meta} . During this time, the value of the output is unknown. It may go to a steady state 1, a steady state 0 or toggle uncontrollably.

④ After coming out of its metastable state, the D-Flip-Flop output will go to one of two stable states, Q=0 or Q=1. The final resting state is random and unknown.


Improvisations

   


Improvisations : Overriding the clock


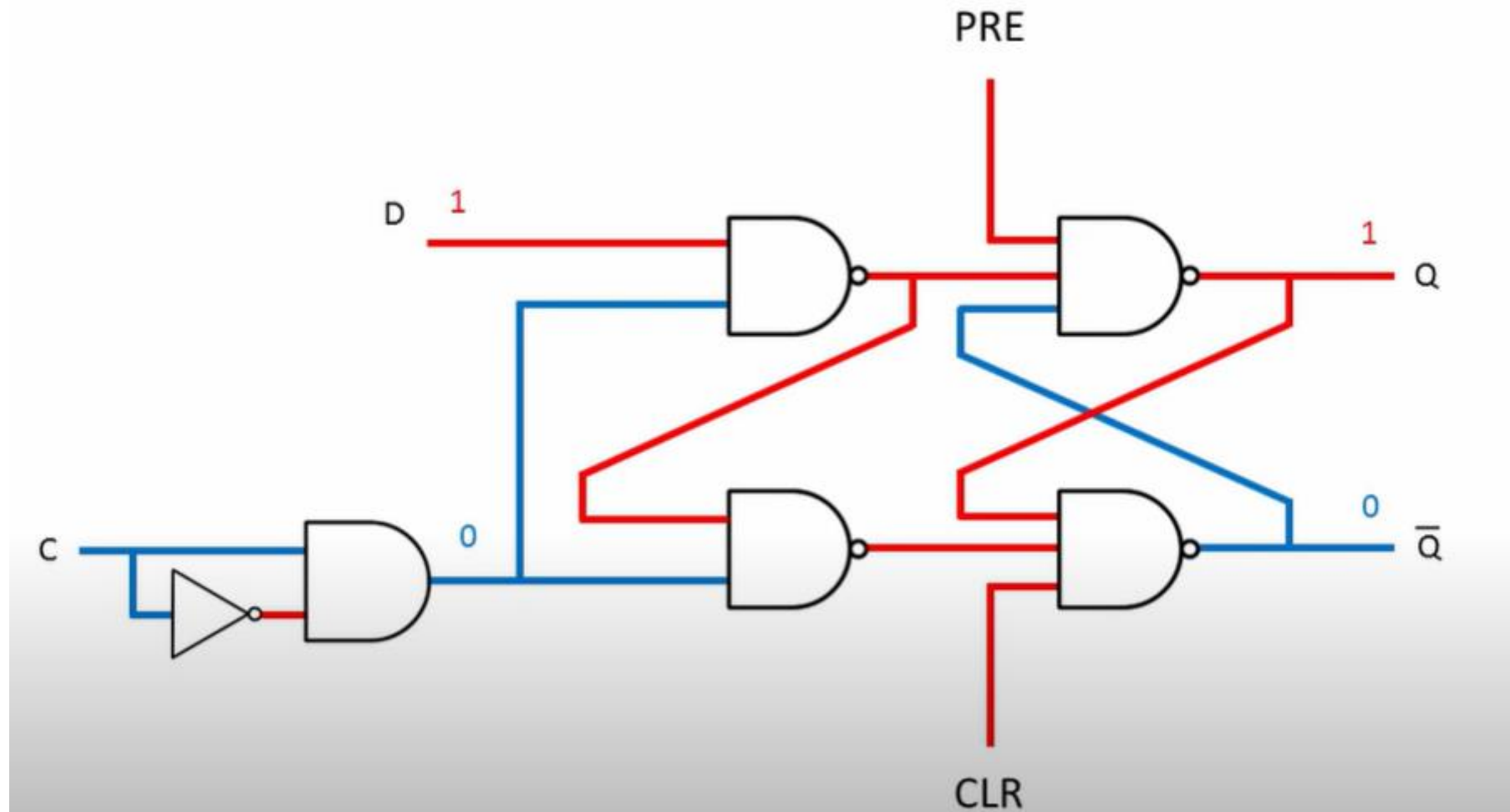




A Clocked D Latch with Preset and Clear

 



The problem of synchronization

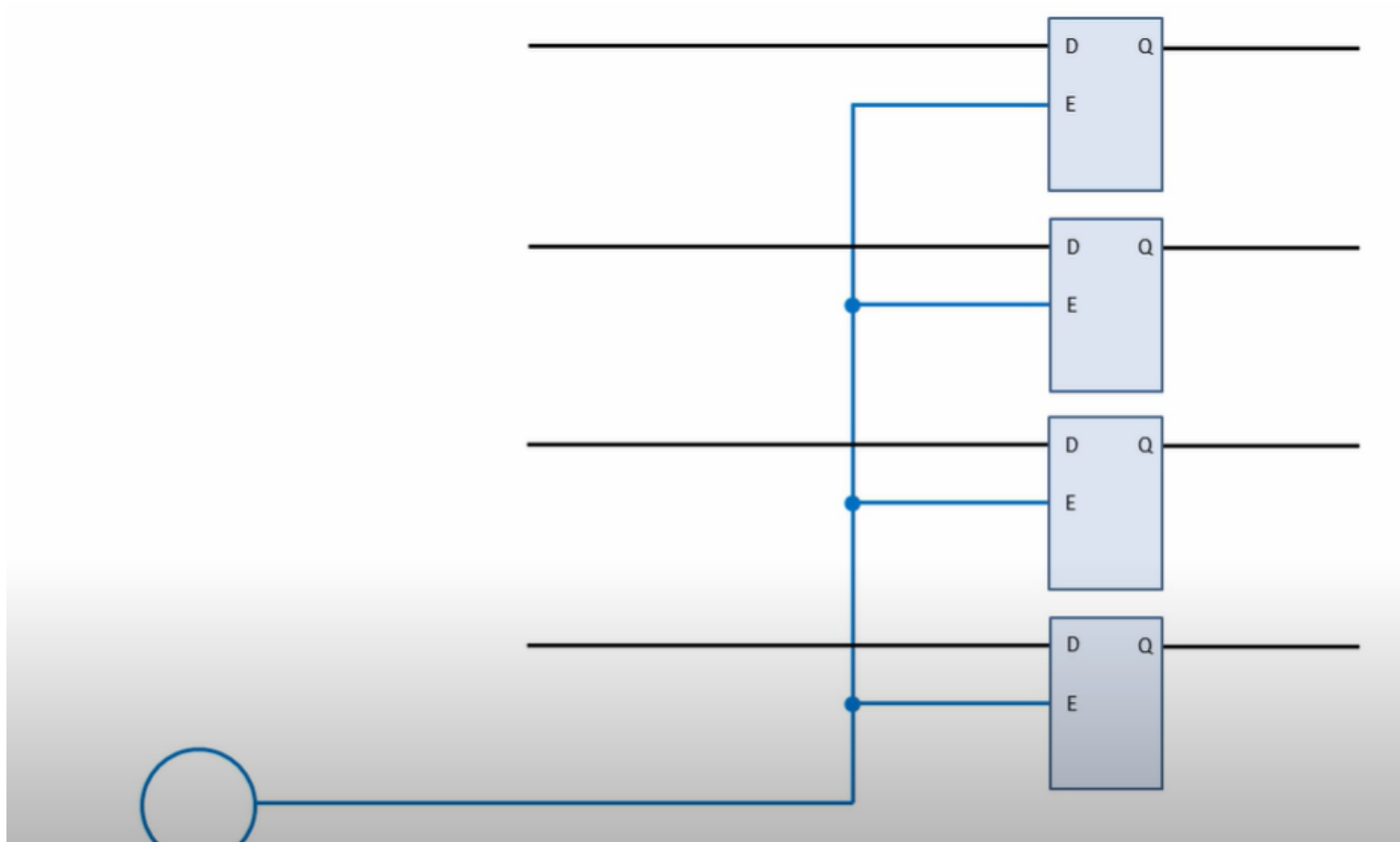

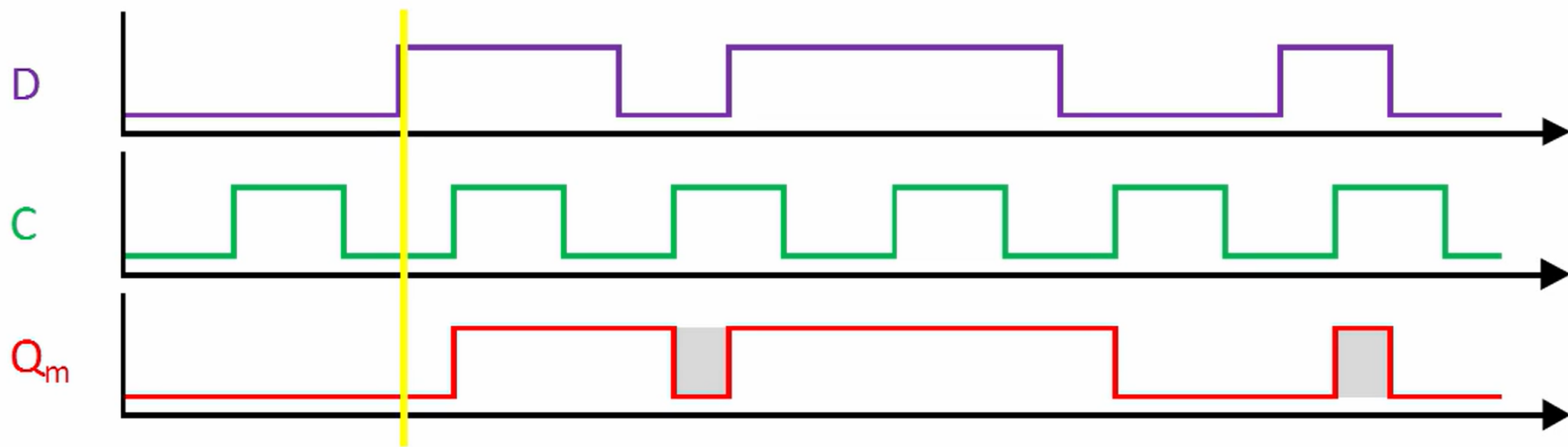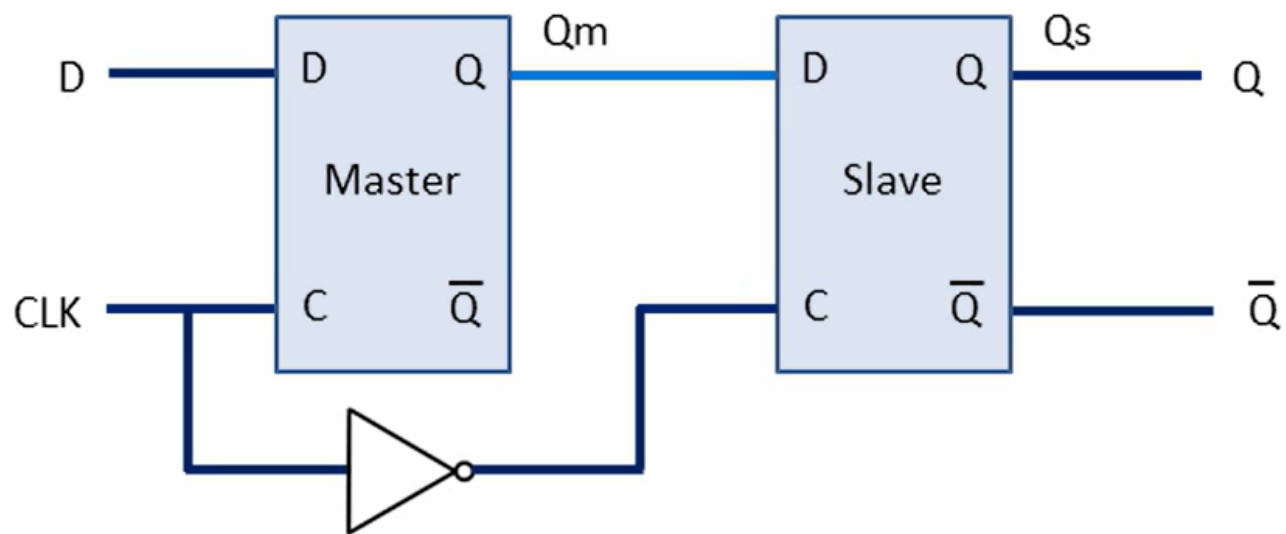

 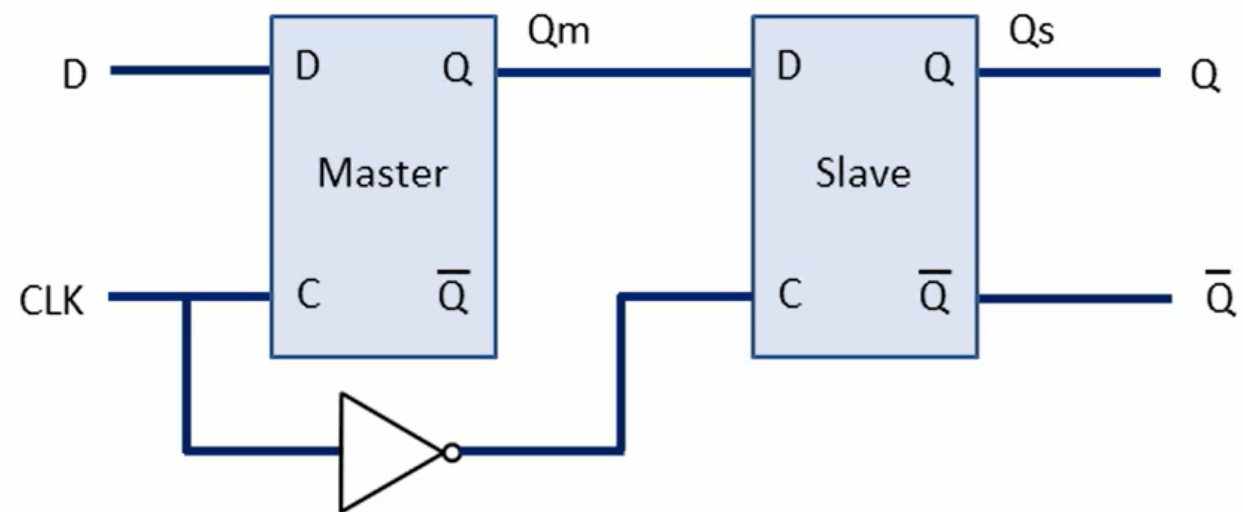

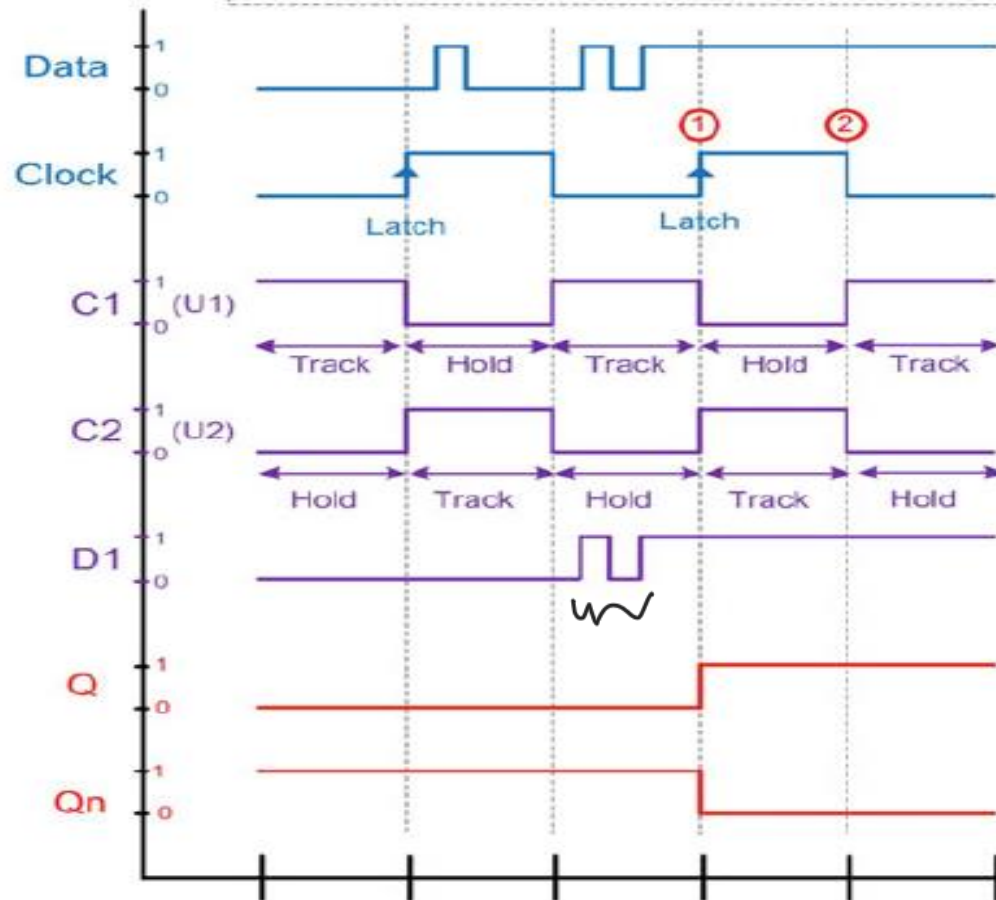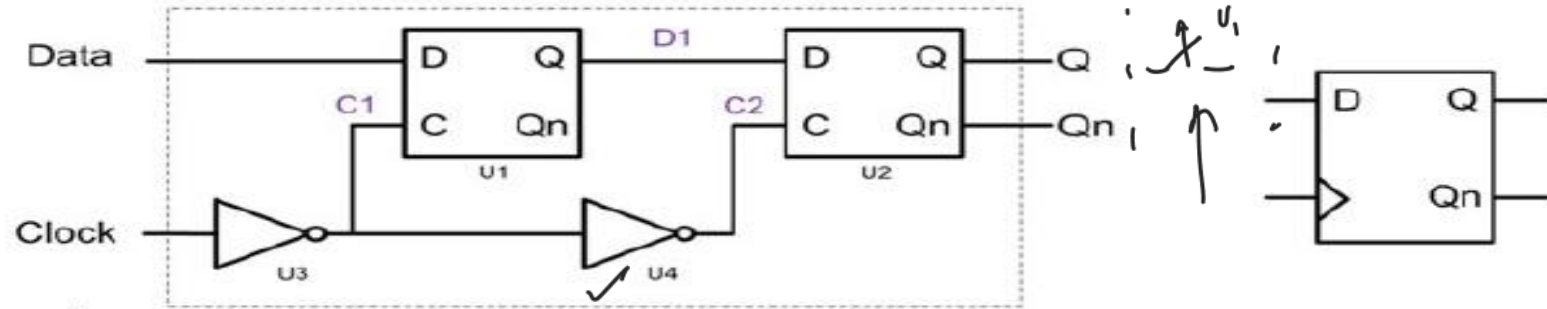D-Flip-Flop (Rising Edge Triggered) Timing Diagram



- ① On this rising edge of clock, Q is updated with the value of D (Q=1).


To accomplish this, U1 goes into hold mode when the clock goes HIGH, which stores the input 1. U2 goes into track mode, passing the 1 to the output Q. This configuration keeps Q=1 for the first part of the clock cycle.

- ② When the clock goes LOW, U2 goes into hold mode, which stores the 1 from U1 and drives Q=1 for the rest of the clock period.

U1 goes into track mode to get ready for the next rising edge of the clock.


D-Flip-Flop with Asynchronous Reset and Preset

D-Flip-Flop with Active LOW Reset

 


\bar{R}	Clk	D	Q	Qn	
0	X	X	0	1	Reset
1	0	X	Last Q	Last Qn	Store
1	1	X	Last Q	Last Qn	Store
1	\bar{f}	0	0	1	Update
1	\bar{f}	1	1	0	Update

 D-Flip-Flop with Active LOW Reset and Active LOW Preset




\bar{R}	\bar{P}	Clk	D	Q	Qn	
0	X	X	X	0	1	Reset
1	0	X	X	1	0	Preset
1	1	0	X	Last Q	Last Qn	Store
1	1	1	X	Last Q	Last Qn	Store
1	1	\bar{f}	0	0	1	Update
1	1	\bar{f}	1	1	0	Update

D-Flip-Flop with Synchronous Enable

 


\bar{R}	\bar{P}	Clk	EN	D	Q	Qn	
0	X	X	X	X	0	1	Reset
1	0	X	X	X	1	0	Preset
1	1	0	X	X	Last Q	Last Qn	Store
1	1	1	X	X	Last Q	Last Qn	Store
1	1	f	0	X	Last Q	Last Qn	Disabled (ignore clock)
1	1	f	1	0	0	1	Update
1	1	f	1	1	1	0	Update

Toggle Flop Clock Frequency Divider

 


 Optional Symbol for a Toggle-Flop or "T-Flip-Flop"



T-


$$f = \frac{1}{T}$$

 

① Q and Qn will always be at opposite logic values.

② When a rising edge of a clock occurs, Q will be updated with the value present on D. Since in this configuration the value on D will always be the opposite of the current value of Q, the outputs will toggle. The outputs will change, or toggle, every time there is a rising edge on the clock. This has the effect of creating a square wave on the output that has $\frac{1}{2}$ the frequency of the clock.

3-Bit Ripple Counter

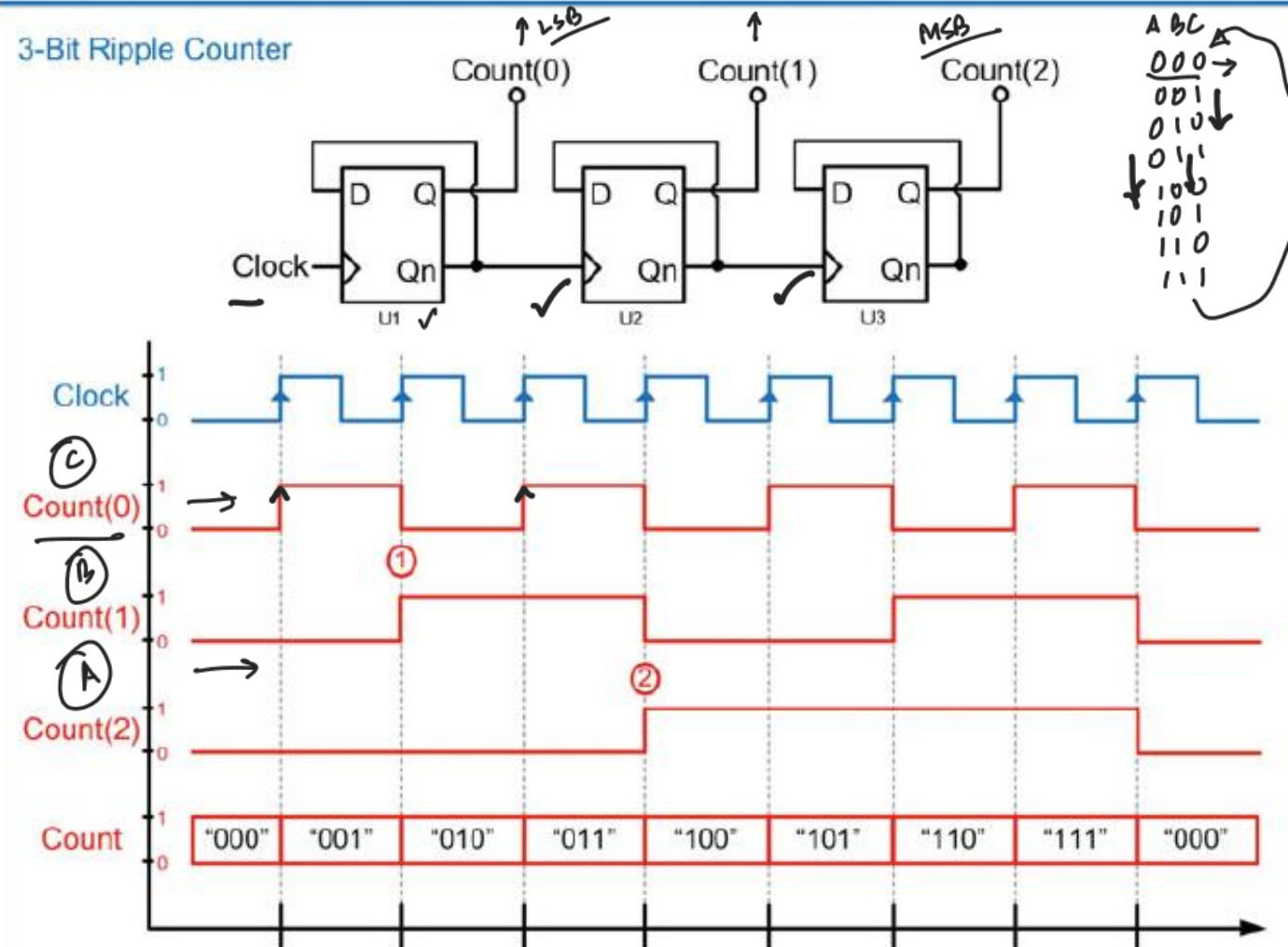

- ① When the Q output of U1 transitions from a 1 to 0, the Qn output of U1 transitions from a 0 to 1, thus producing a rising edge that is used to clock U2. This rising edge causes U2 to toggle.
- ② When the Q output of U2 transitions from a 1 to 0, the Qn output of U2 transitions from a 0 to 1, thus producing a rising edge that is used to clock U3. This rising edge causes U3 to toggle.

Two Problems


- Analysis
- Design

Analysis of Sequential Circuits


- Steps :

Circuit diagram \rightarrow Equations – State table \rightarrow State diagram

Step 1: Circuit

 

Step 2: Equations

 

Input Equation:


$$\underline{D_A = A \oplus x \oplus y}$$

State Equation:

$$\underline{A(t + 1) = A \oplus x \oplus y}$$

$A(t)$

Step 3: State Transition Table

 

Input Equation:

$$D_A = A \oplus x \oplus y$$

State Equation:


$$A(t + 1) = A \oplus x \oplus y$$

✓

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

↓

Step 4: State Transition Diagram

 


Input Equation:

$$D_A = A \oplus x \oplus y$$

State Equation:

$$A(t + 1) = A \oplus x \oplus y$$

 

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Design Problem


- Steps:
 - Word Description
 - State Transition Diagram
 - State Transition Table
 - K-maps for Sequence Detector
 - Logic/Circuit Diagram

Step 1: Word Description

We wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*).


Step 2: State Transition Diagram

 We wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*).



Step 3: State Transition Table

 
We wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*).




Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Step 4: K-Maps

 
We wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*).




$$D_A = Ax + Bx$$

 

$$D_B = Ax + B'x$$

 

$$y = AB$$

 

inputs

Present State		Input		Next State		Output
A	B			A	B	
0	0	0		0	0	0
0	0	1		0	1	0
0	1	0		0	0	0
0	1	1		1	0	0
1	0	0		0	0	0
1	0	1		1	1	0
1	1	0		0	0	1
1	1	1		1	1	1

Step 5: The Logic Diagram of The Sequence Detector

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = \underline{AB}$$

