




# Sequential Circuits

Practice Problems

Design a 3-bit counter using D flip-flops which counts in the sequence 001, 011, 010, 110, 111, 101, 100, (repeat), 001, 011, ...


What will happen if the counter is started in the state 000?


$CBA$	$C^+B^+A^+$
0 0 0	X X X
0 0 1	0 1 1
0 1 0	1 1 0
0 1 1	0 1 0
1 0 0	0 0 1
1 0 1	1 0 0
1 1 0	1 1 1
1 1 1	1 0 1

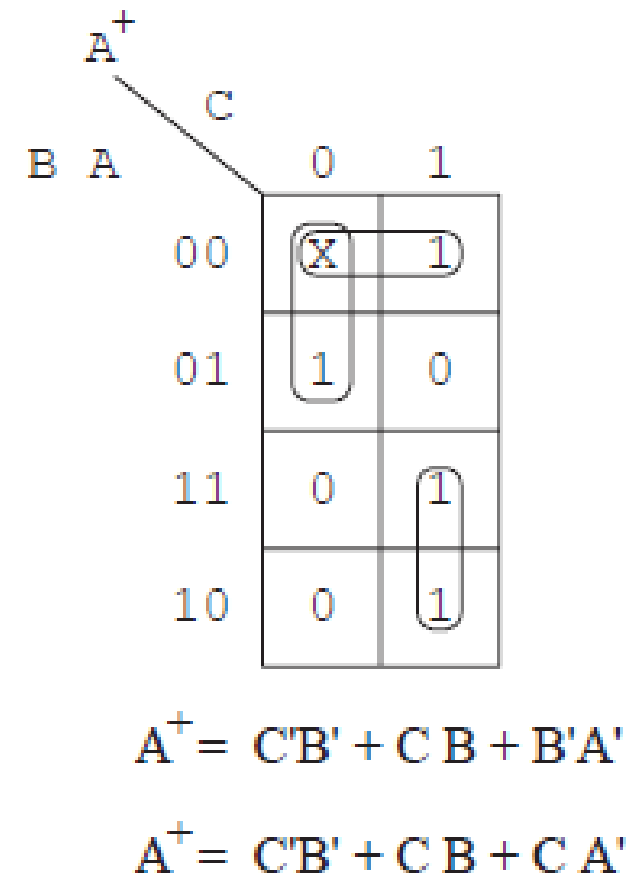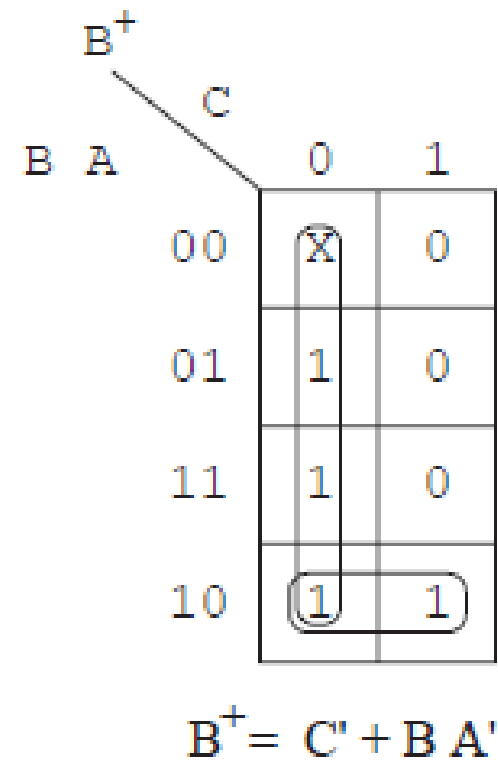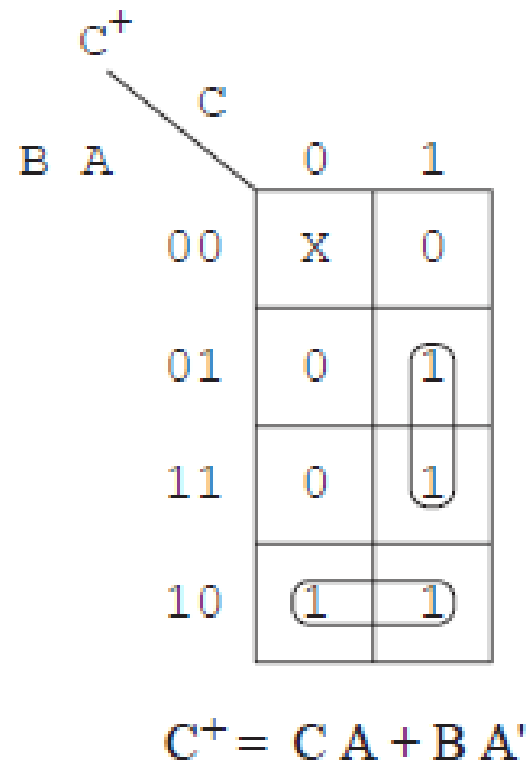

For D flip-flop: 000 goes to 011 because  $D_C D_B D_A = 011$

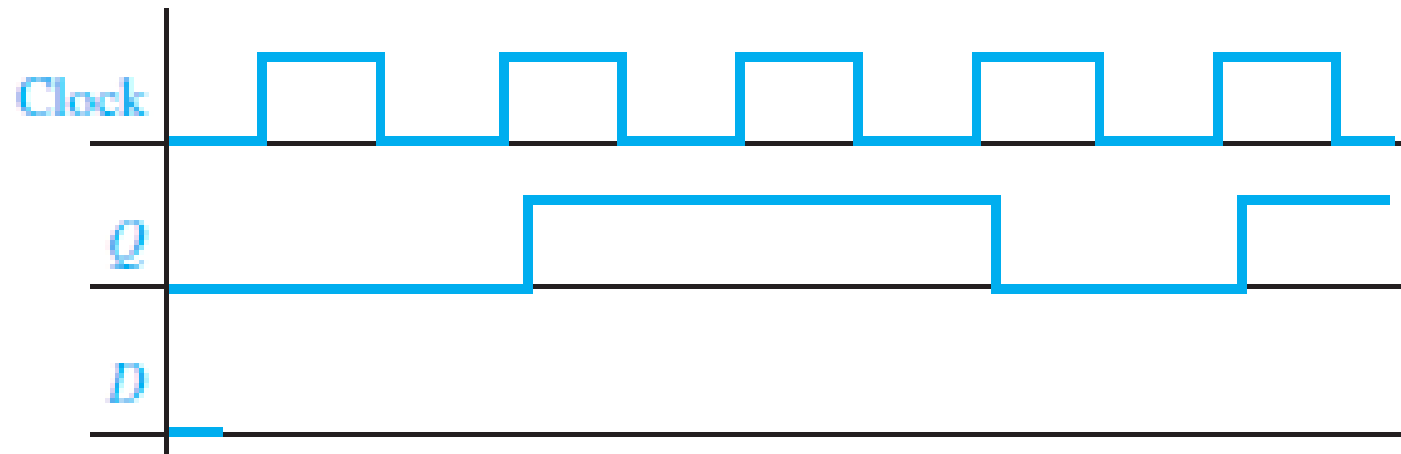Find the input for a rising-edge-triggered D flip-flop that would produce the output  $Q$  as shown. Fill in the timing diagram.



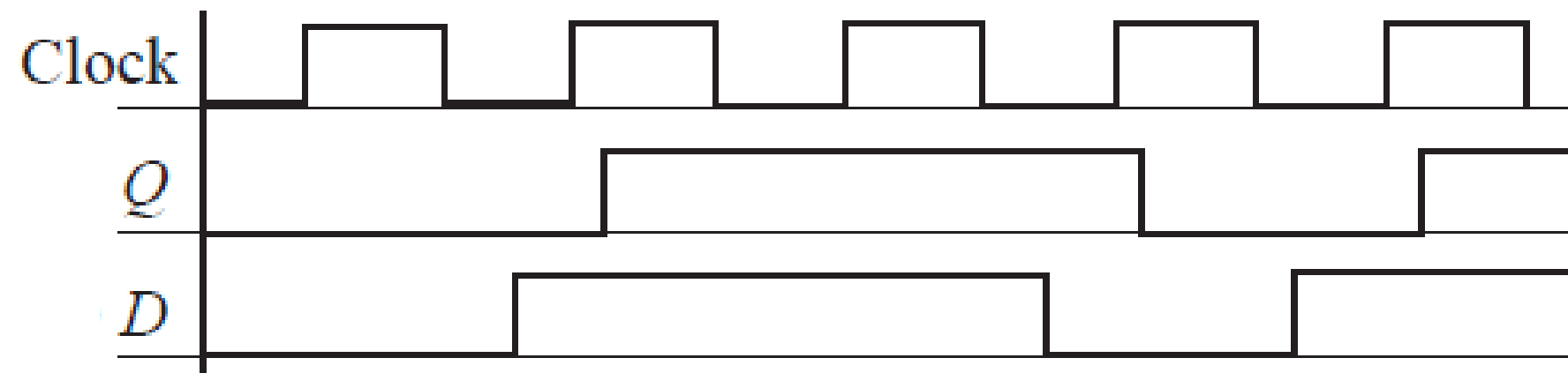


# Design problem

- Sequence detector: any input sequence ending with 101 produces output  $Z = 1$  coincident with the last 1

$X =$  0 0 1 1 0 1 1 0 0 1 0 1 0 1 0 0  
 $Z =$  0 0 0 0 0 1 0 0 0 0 0 1 0 1 0 0  
(time: 0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15)

# Mealy Machine

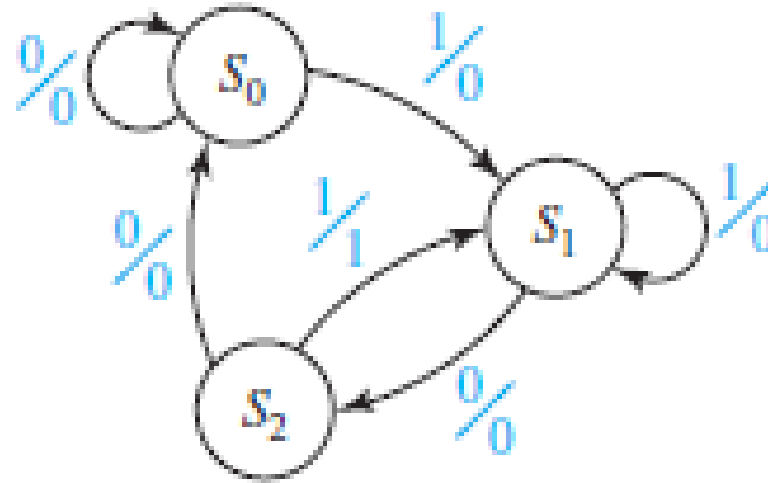

Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
S <sub>1</sub>	S <sub>2</sub>	S <sub>1</sub>	0	0
S <sub>2</sub>	S <sub>0</sub>	S <sub>1</sub>	0	1

AB	A <sup>+</sup> B <sup>+</sup>		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

X \ AB	0	1
00	0	0
01	1	0
11	X	X
10	0	0


$$A^+ = X'B$$

X \ AB	0	1
00	0	1
01	0	1
11	X	X
10	0	1


$$B^+ = X$$

X \ AB	0	1
00	0	0
01	0	0
11	X	X
10	0	1

$$Z = XA$$

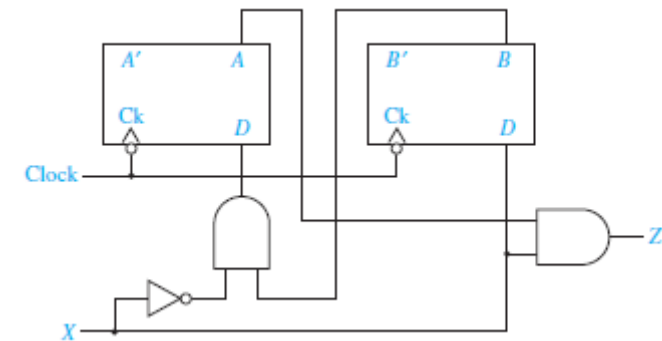

# Moore Machine

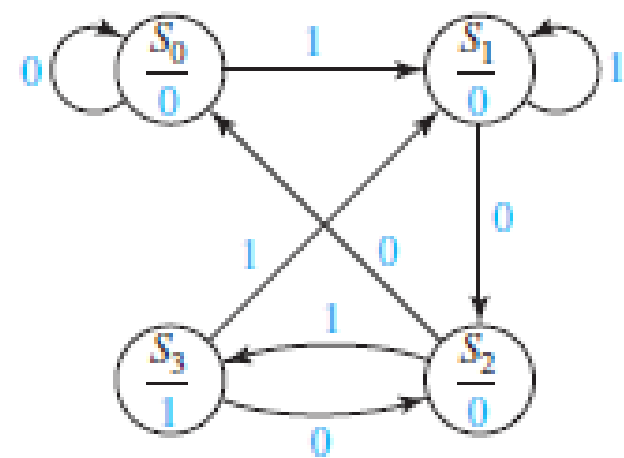

Present State	Next State		Present Output(Z)
	X = 0	X = 1	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0
S <sub>1</sub>	S <sub>2</sub>	S <sub>1</sub>	0
S <sub>2</sub>	S <sub>0</sub>	S <sub>3</sub>	0
S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	1

AB	A <sup>+</sup> B <sup>+</sup>		Z
	X = 0	X = 1	
00	00	01	0
01	11	01	0
11	00	10	0
10	11	01	1



Is this Mealy or Moore?

