

## EE1100 - Diodes and Op-amps

### Problem 1

Consider the following circuit. Assume the op-amp is ideal and the diode follows the constant voltage-drop model ( $V_D = 0.7$  V when forward-biased). Calculate  $V_0$  if  $V_i = +1$  V

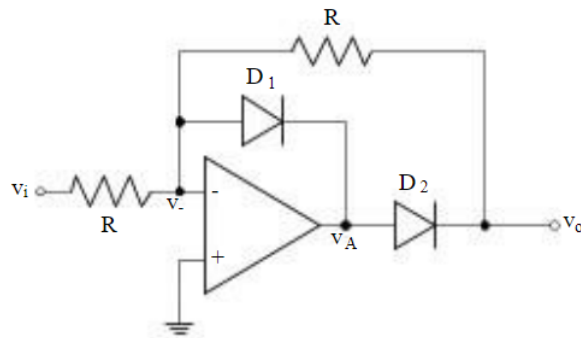


Figure 1: Circuit for Problem 1

### Problem 2

In the figure shown below, the input offset voltage and input offset current are  $4\text{mV}$  and  $150\text{nA}$  respectively. Find the total output offset voltage.

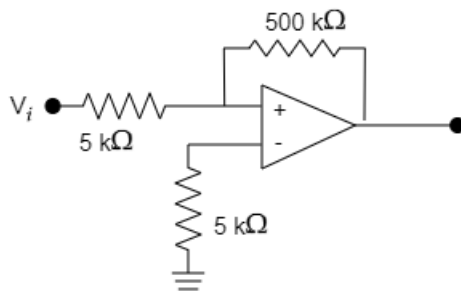


Figure 2: Circuit for Problem 2

Ans: 479mV

### Problem 3

Derive the expression for output voltage in the circuit below

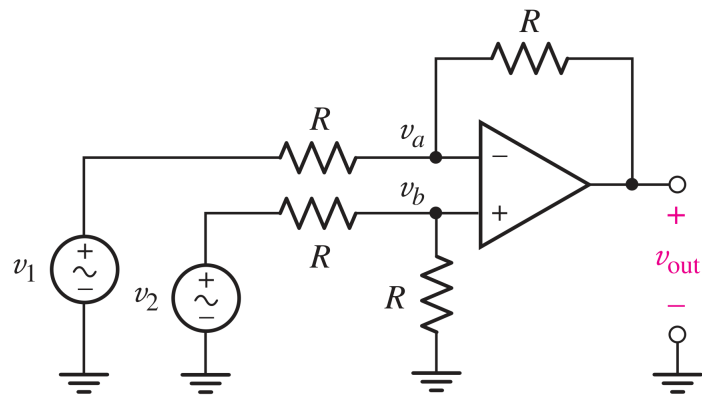


Figure 3: Problem 3