

EE1100  
Basic Electrical Engineering  
Tutorial 1

February 2024

**Problem 1**

In the circuit shown below, Find the value of  $R_L$  so that power transferred to  $R_L$  is maximum.

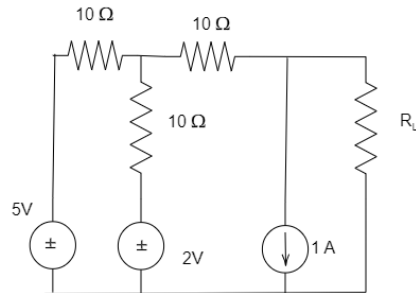


Figure 1: Circuit 1

**Problem 2**

In the given circuit, as shown in Fig 2. Find the current through the  $1\Omega$  resistance. *Hint:* Try to solve it using source transformation.

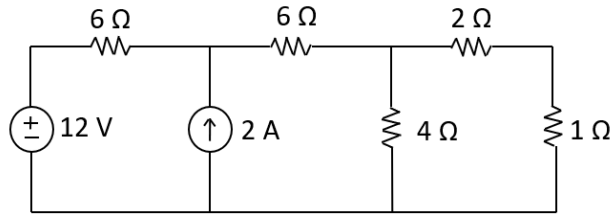


Figure 2: Circuit 2

### Problem 3

Find the current through the  $10\Omega$  resistance in the given circuit Fig 3. Solve it using Norton's law.

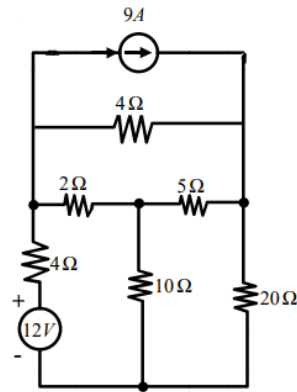


Figure 3: Circuit 3

### Problem 4

Using Mesh analysis, find the voltage  $V_x$  and the currents  $I_x$  and  $I_y$  in the given electric circuit 4.

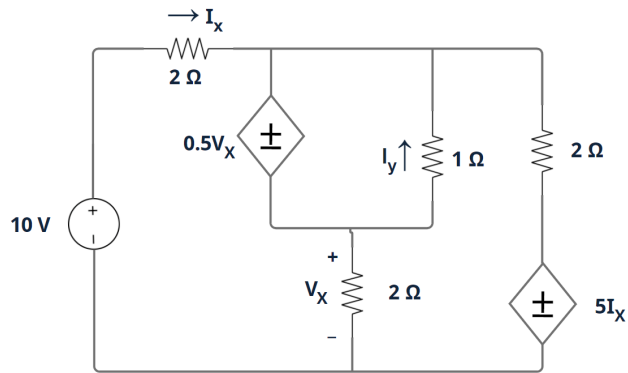


Figure 4: Circuit 4

## Problem 5

Find the current  $i$ , using Thevenin theorem

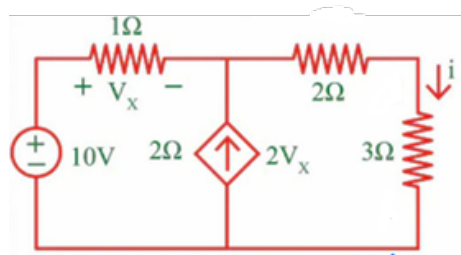


Figure 5: Circuit 5

## Problem 6

Find the current through the load resistor (1K means  $1\text{K}\Omega = 1000\Omega$ )

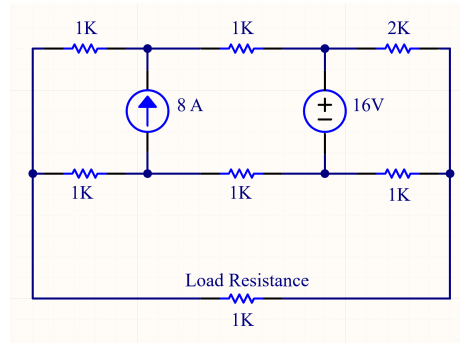


Figure 6: Circuit 6