

Tutorial 6 EE1100

Resonance

Problem 1

In the circuit shown, find the amplitude of the sinusoidal voltage across the capacitor when the circuit is at resonance condition.

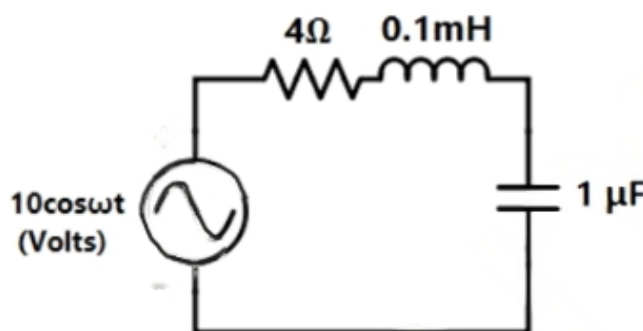


Figure 1: Circuit 1

Problem 2

For the given circuit 2, find the cut-off frequencies

Ans: $\Delta f_1 = 1.256$ MHz; $\Delta f_2 = 1.244$ MHz

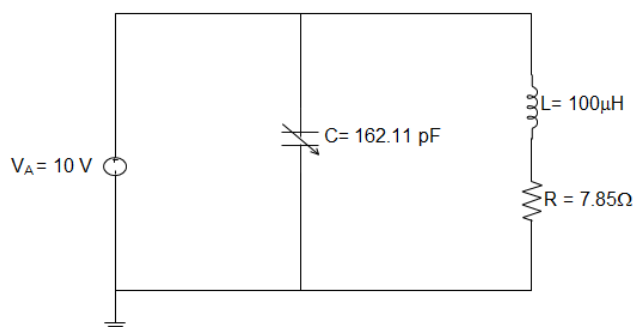


Figure 2: Circuit 2

Problem 3

For the network shown in figure 3, Find input impedance ($Z_{in}(j\omega)$) and the resonant frequency.

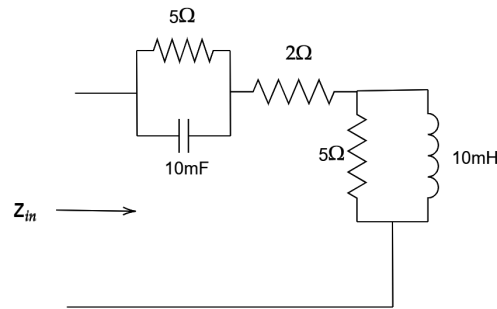


Figure 3: Circuit 3

Ans: $\omega = 100 \text{ rad/sec}$

Problem 4

Consider a parallel RLC circuit such that $L = 2 \text{ mH}$, $Q = 5$, and $C = 10 \text{ nF}$. Determine the value of R and the magnitude of the steady-state admittance at $0.1\omega_0$, ω_0 , and $1.1\omega_0$, where ω_0 is the resonant frequency in rad/sec, and Q is the quality factor.

Ans: $|Y(0.9\omega_0)| = 6.504 * 10^{-4} S$, $|Y(\omega_0)| = 4.472 * 10^{-4} S$, $|Y(1.1\omega_0)| = 6.182 * 10^{-4} S$

Problem 5

A certain series resonant circuit has $f_0 = 500 \text{ Hz}$, $Q_0 = 10$ and $XL = 500 \text{ ohm}$ at resonance.

a). Find R , L , C

b). If a source $V_s = 1 \text{ V}$ is connected in series with the circuit, find V_c at $f = 450 \text{ Hz}$.

Ans:- $R = 50 \text{ ohm}$, $L = 0.159 \text{ H}$, $C = 0.6372 \mu\text{F}$ $V_c = 4.755 \text{ V}$

Problem 6

The voltmeter in the circuit 4 is reading zero volts. Find the value of R_x and L_x .

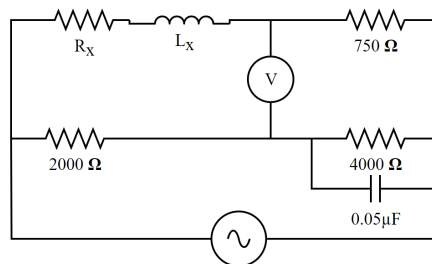


Figure 4: Circuit 4

Answer: 375Ω , $75 \mu\text{H}$