

## Tutorial 4

### Problem 1

In the circuit shown in Fig 1, find the phase angle difference between  $I_1$ ,  $I_2$  in degrees.

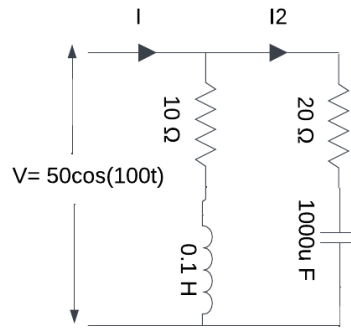


Figure 1: Fig 1

Ans:  $45^\circ$

### Problem 2

From the circuit shown find the instantaneous current  $i_1(t)$ .

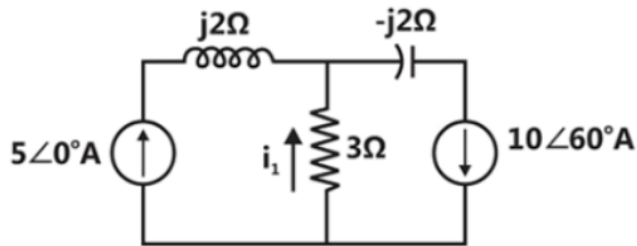


Figure 2: Circuit 2

Ans:  $5 * \sqrt{3} \angle 90$

### Problem 3

Represent all the currents in circuit 3 in a phasor diagram.

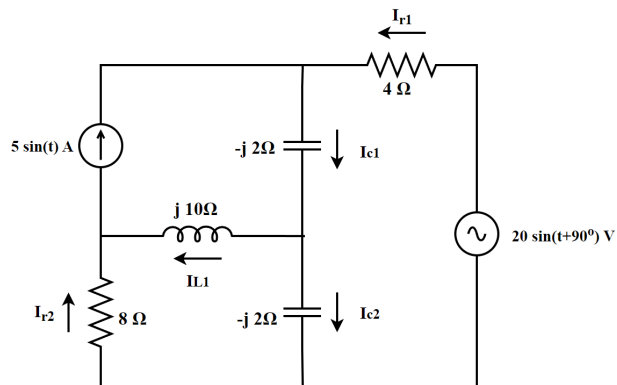


Figure 3: Circuit 3

### Problem 4

Find  $V_3$  in the given circuit Fig 4. Given  $R_1 = R_2 = R_3 = 1\Omega$ ,  $R_4 = 2\Omega$ ,  $X_L = 2\Omega$  and  $X_C = 2\Omega$

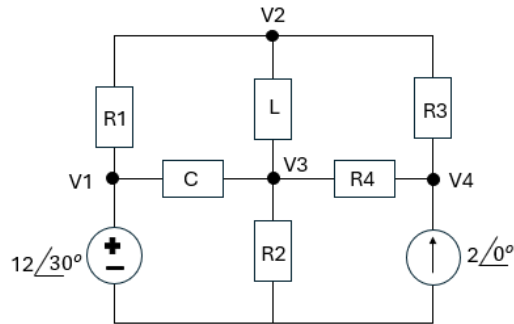


Figure 4: Circuit 4

## Problem 5

Find the input impedance  $Z_{in}$  that would be measured between terminals: (a) a and g; (b) b and g; (c) a and b

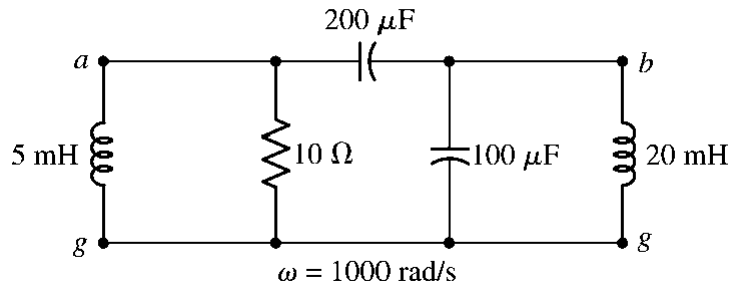


Figure 5: Circuit for problem 5

Ans:  $2.81 + j4.49\Omega$ ,  $1.798 - j1.124\Omega$ ,  $0.1124 - j3.82\Omega$