

## Tutorial 5

### EE1100

#### Problem 1

A square wave current source of amplitude 200 mA is passed through a capacitor of  $100 \mu\text{F}$ . Time period of the positive and negative half cycles is 100 ms. Plot the voltage waveform, find its average and RMS values.

Ans: Average voltage = 100 V; RMS voltage = 115.47 V

#### Problem 2

The current through an inductor in series with 10 ohm resistor is given by  $i(t) = 3 + 4\sin(100t+45) + 4\sin(300t+60)$  A . Find the RMS of current through the resistor .

#### Problem 3

The waveform shown in Fig.1 is a half-wave rectified sine wave. Find the RM value and the amount of average power dissipated in a  $10\text{-}\Omega$  resistor.

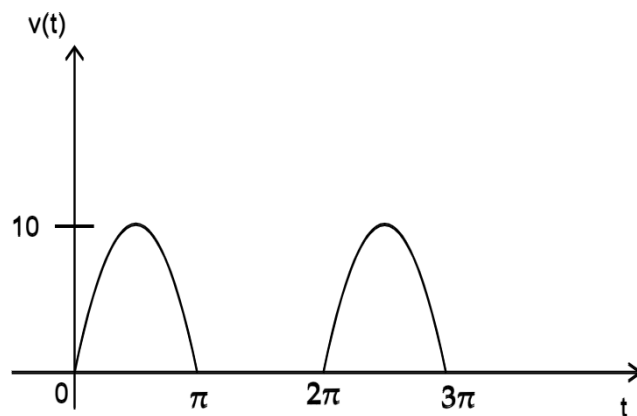


Figure 1: For problem 3

Ans:  $V_{rms} = 5\text{V}$ ,  $P = 2.5\text{W}$

## Problem 4

Find the RMS and average values of the currents given below, assuming all three currents are periodic and have a period of  $200\mu s$ :

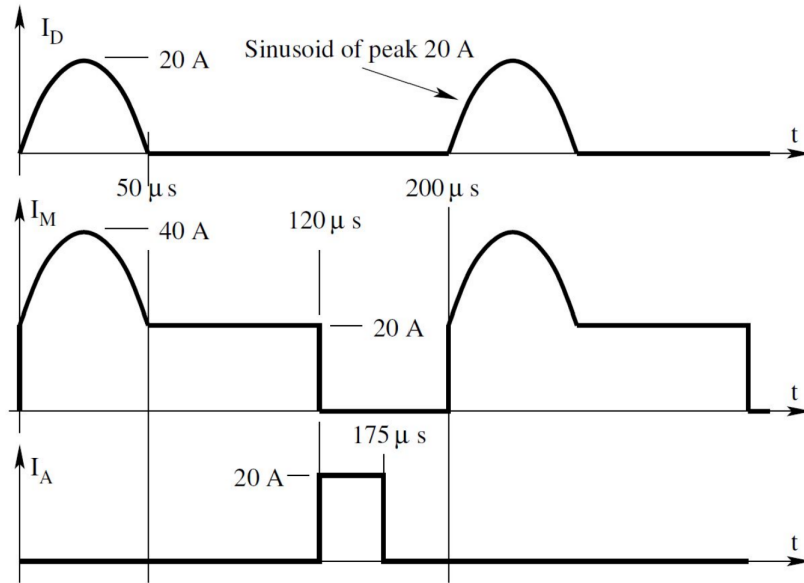


Figure 2: Waveforms for problem 4

Answers:

$$\begin{aligned} I_{d-avg} &= 3.183A, & I_{d-rms} &= 7.071A, \\ I_{M-avg} &= 15.183A, & I_{M-rms} &= 20.37A, \\ I_{A-avg} &= 5.5A, & I_{A-rms} &= 10.488A \end{aligned}$$

## Problem 5.(a)

Find the rms value of figure shown. Ans:- 64.42V

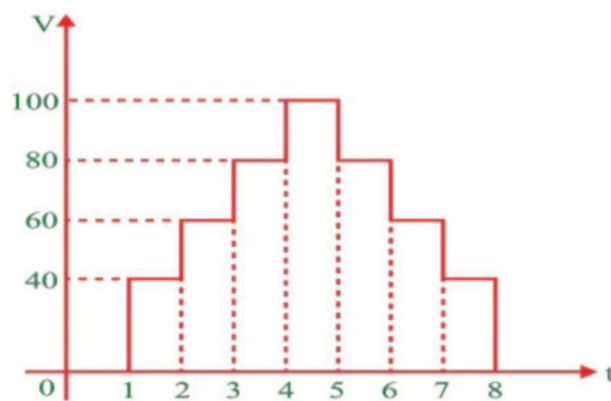


Figure 3: 5 (a)

## Problem 5.(b)

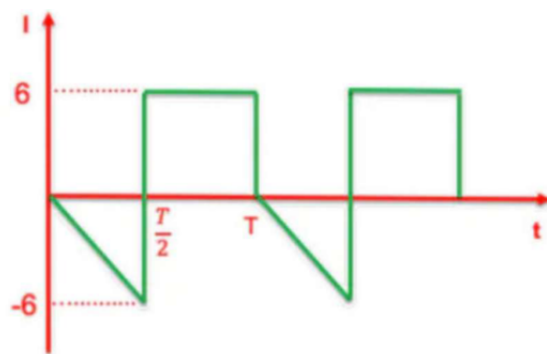


Figure 4: 5 (b)

ANS:- 4.89

## Problem 6

A 1000 W load is connected to a sinusoidal voltage source of peak amplitude 200 V which draws a current with a peak amplitude of 10 A as shown in figure 5. Find the total power factor of the source.

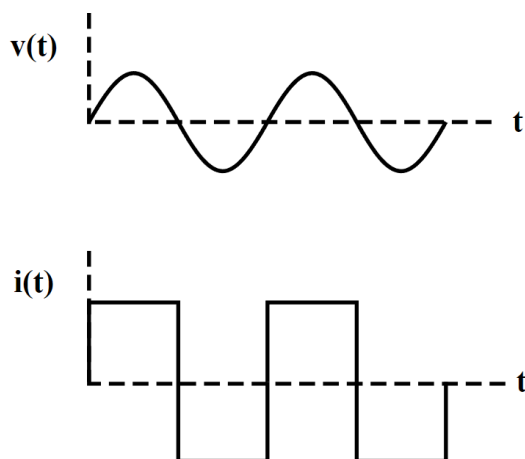


Figure 5:

Ans: 0.866